

APPLICATION NOTES

Premier Magnetics' TSD-825 Switch Mode Transformer was designed for use with Power Integrations, Inc. TOP221P three terminal off-line PWM switching regulator in the Flyback Buck-Boost circuit configuration. This conversion topology can provide isolated multiple outputs with efficiencies up to 90%. Premiers' TSD-825 transformer has been optimized to provide maximum power throughput.

The TOP2XX series from Power Integrations, Inc. are self contained 100KHz three terminal voltage controlled PWM switching regulators. This series contains all necessary functions for an off-line switched mode control DC power source. These switching regulators provide a very simple solution to off-line designs. The inductors and transformer used with the PWR-TOPXXX are critical to the performance of the circuit. They define the overall efficiency, output power and overall physical size.

Below is a universal input, 4 watt application circuit utilizing Power Integrations TOP221 switching regulator in the flyback buck-boost configuration. This circuit provides +12Vdc at 300mA continuous and is capable of 400mA peak for short periods of time. This circuit represents the lowest cost implementation and utilizes the bias winding for feedback control. As such the line & load regulation are worse than that which could be achieved by utilizing an opto-coupler to sense the actual outputs. The component values listed are intended for reference purposes only. Resistor R1 may be adjusted up to 100 Ohms and down to 10 Ohms. As R1 increases in value the output voltages will increase, and vice-versa, thus allowing some fine adjustment on the initial output voltage. The EMI/RFI capacitors C7 & C8 are shown for reference but may not be needed to meet EMI/RFI emmision specifications.

FIGURE 3: TYPICAL APPLICATION CIRCUIT

